

Overview: Digital Circuits

- * Logic Signals
- * Logic Families
- * IC Fabrication
- * CMOS Logic




Chapters 1 & 3 – “Digital Design: Principles and Practices” book

Note: *Some pictures in this topic were extracted from the web.*

Logic Signals & Gates

- Logical signals are often called *low* and *high*, to refer to the values 0 and 1 (not necessarily in this order!).
 - Also, *low* often corresponds to algebraically lower voltages while *high* corresponds to higher voltages.
 - Types of logic:
 - *Positive Logic* assigns 0 to *low* and 1 to *high*.
 - *Negative Logic* assigns 0 to *high* and 1 to *low*.
- The most natural type.
- Not often used.

Positive and Negative Logic

 

- Truth tables:**


Negative

Positive

A	B	X
1	1	0
1	0	1
0	1	1
0	0	1

A	B	X
0 V	0 V	5 V
0 V	5 V	0 V
5 V	0 V	0 V
5 V	5 V	0 V

A	B	X
0	0	1
0	1	0
1	0	0
1	1	0

 

Logic Value	Voltage Level
0	L
1	H

Logic Value	Voltage Level
0	H
1	L

Signal Variation

- A **binary value represents a wide range of voltages**, so digital signals are highly immune to voltage variation!
- **Example** (*typical ranges*):
 - For a CMOS gate, its *high* ranges from *3.5 V* to *5.0 V* while its *low* ranges from *0 V* to *1.5 V*.
- **Note:** *CMOS* means Complementary MOS, and *MOS* (short for Metal-Oxide Semiconductor Field-Effect) is a type of transistor with low power consumption and high level of integration.

Operation of Logic Gates

- “Ideal” Logic Gates:
 - *Input* and *output voltages* are at either the **high** or the **low** value specified for the *logic family*.
 - *Inputs* draw no current from whatever drives them, and *outputs* can supply as much current as necessary for whatever follows.
 - *Any change to an input* will **immediately** be *reflected on the output*.



Real logic gates operate under several restrictions!

Overview: Digital Circuits

- * Logic Signals
- * Logic Families
- * IC Fabrication
- * CMOS Logic

More *detailed information* at (especially **important** if you are taking the 3rd year courses **EBU5335** and **EBU5475**):
http://www.opamp-electronics.com/tutorials/digital_theory_ch_003.htm.




Chapters 1 & 3 – “Digital Design: Principles and Practices” book

Logic Families



There are *other logic families* and *sub-families* (but *out of scope* here).

- **Logic family**: Collection of different IC chips that have similar input, output, and internal circuit characteristics, but perform different logic functions.
 - Thus, **chips from different logic families may not be compatible**.
- Two **most common logic families**:
 - *Transistor-Transistor Logic* (TTL), and
 - *Complementary Metal-Oxide Semiconductor field effect transistor* (CMOS).
- **Differences between TTL and CMOS**: materials, fabrication methods, and electrical behaviours.

 

Logic Levels: TTL & CMOS

- **CMOS** (*Complementary MOS*): built on MOS transistors.
 - (*) *Logic values*: (*) *Typical values only*.
0 → voltages: **0-1.5 Volts**; **1** → voltages: **3.5-5.0 Volts**.
 - Used by most **large-scale ICs** (e.g., microprocessors and memory).
- **TTL** (*Transistor-Transistor Logic*): built on bipolar junction transistors.
 - (*) *Logic values*:
0 → voltages: **0-0.8 Volts**; **1** → voltages: **2.0-5.0 Volts**.
 - Once used for small to medium-scale applications, now usually replaced by CMOS devices. **TTL components can still be found in university labs.**

Logic Family Parameters


- Characteristics of digital logic families are compared by analysing the circuit of the basic gate in each family, using *parameters*:
 - Fan-out, Fan-in (measured in *number of inputs*)
 - Power Dissipation (measured in *watts*): *power consumed by the gate* that must be available from the power supply.
 - Propagation Delay (measured in *seconds*)
 - Noise margin (measured in *volts*)

	T_p (ns)	P (mW)	Noise Margin (mV)	Fan-out
TTL	9	10	400 (OH); 400 (OL)	10
CMOS	18	0.01 (static)	1050 (OH); 1340 (OL)	≤ 50

T_p : propagation delay

P : power dissipation per gate


Logic Levels

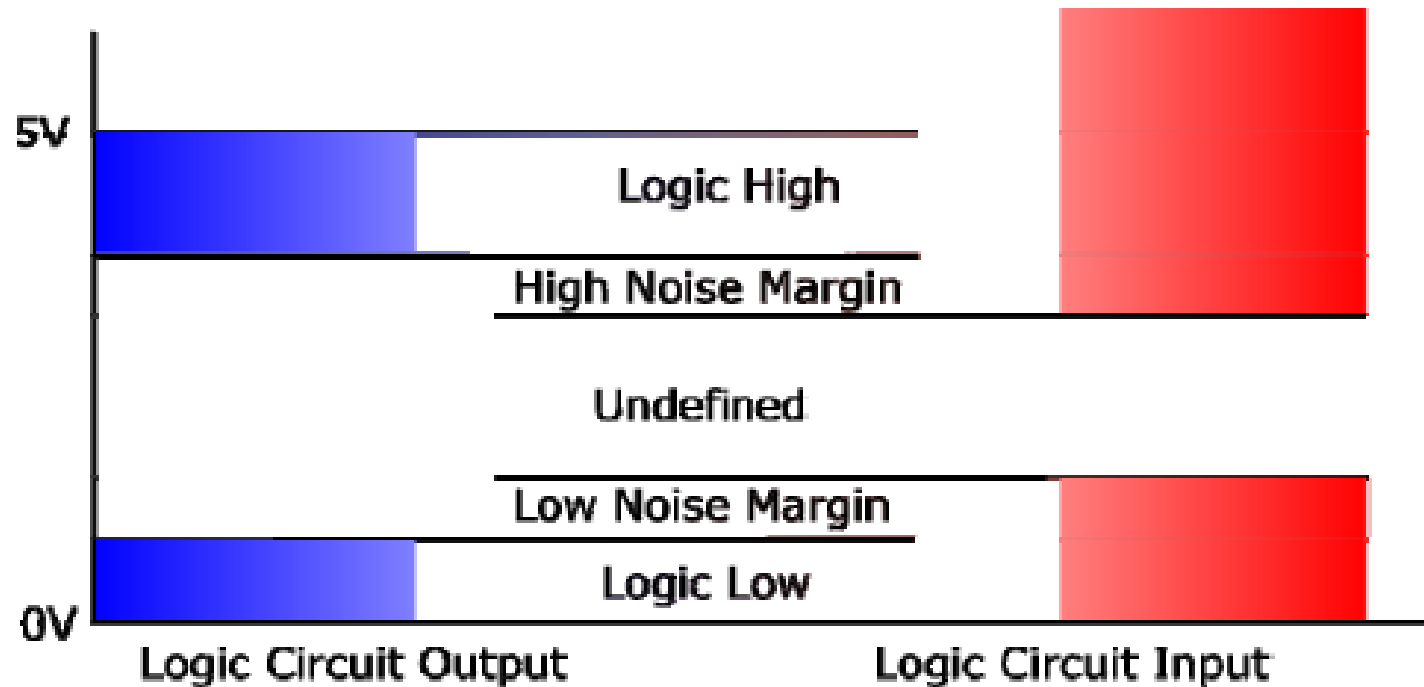

- *Different logic families* may have different logic levels.
- **Noise Margin**: *maximum external noise voltage* that can be added to an input signal *without causing an undesirable change in the circuit output*.

Fan-in & Fan-out: Definition

 - **Fan-in** refers to the number of inputs a gate can have in a particular logic family.
 - In other words, it's the number of inputs that a gate can practically have.
- **Fan-out** refers to the maximum number of logic inputs that an output can drive reliably.
 - It depends not only on the *characteristics of the output*, but also depends on the *characteristics of the input*.



Fan-in & Fan-out: Characteristics

- **Fan-in:**

- Too many inputs for a gate may lead to significant delay.
- The number of inputs on most CMOS gates is limited to between 4 and 6.
- Gates with a large number of inputs can be made faster and efficient by cascading gates with fewer inputs.

- **Fan-out:**

- If too much fan-out is connected to an output, the DC noise margin may not be adequate.
- Fan-out may also affect speed.

Impedance (*aka resistance* for very simple circuits)



- **Impedance**: measure of the *overall opposition* of a circuit to **current**.
- **Input impedance** (as “seen” by anything connected to the input of a circuit) should be *at least 10 times higher* than the **output impedance** of the circuit supplying a signal to the input.
 - This is to **avoid** the input *overloading* the source of the signal and reducing the strength (voltage) of the signal by a substantial amount.
- If an **output impedance** is *too high*, it will be unable to supply a sufficiently strong signal to the load because most of the signal’s voltage will be “lost” inside the circuit driving current through the **output impedance**; the load could be e.g., the **input impedance** of another circuit.

Ideal values for **impedance** (i.e., what is assumed when designing circuits at gate and system level of abstraction):

$$Z_{\text{in}} = \infty \quad // \quad Z_{\text{out}} = 0.$$


Unused Inputs

  - Digital devices can only deal with *signals* that have *well defined logic levels* (i.e., a *0* or a *1*).
- *Floating signals* can cause *unpredictable behaviour* in circuits.
- *Pull-up* and *pull-down resistors*: ensure that given no other input, a circuit assumes a default value (i.e., a *1* or a *0*, respectively).



Timing Diagrams

 - Dimensions on which logic circuits work: truth tables & time.
- Timing diagrams: describe how a circuit behaves in response to varying input signals over time.
 - Show that signals do not change between 0 and 1 instantaneously, and there is a transition period between input and output.



Speed, Propagation Delay & Data Sheets

- **Speed limitations:**
 - *Delay encountered by a signal* going through a single gate.
 - *Number of levels* in the circuit.
- **Propagation delay:** the amount of time needed for a change in the input signal to produce a change in the output signal.
- **Data sheet** of a chip (or digital device): specifies the device's logical and electrical characteristics, as well as operating conditions.



To ensure the device works properly, the operating conditions must be satisfied.

Example: Data Sheet

Note: Taken from course textbook (page 98).

Table 3-3 Manufacturer's data sheet for a typical CMOS device, a 54/74HC00 quad NAND gate.

DC ELECTRICAL CHARACTERISTICS OVER OPERATING RANGE

The following conditions apply unless otherwise specified:

Commercial: $T_A = -40^\circ\text{C}$ to $+85^\circ\text{C}$, $V_{CC} = 5.0\text{V} \pm 5\%$; Military: $T_A = -55^\circ\text{C}$ to $+125^\circ\text{C}$, $V_{CC} = 5.0\text{V} \pm 10\%$

Sym.	Parameter	Test Conditions ⁽¹⁾		Min.	Typ. ⁽²⁾	Max.	Unit
V_{IH}	Input HIGH level	Guaranteed logic HIGH level		3.15	—	—	V
V_{IL}	Input LOW level	Guaranteed logic LOW level		—	—	1.35	V
I_{IH}	Input HIGH current	$V_{CC} = \text{Max.}$, $V_i = V_{CC}$		—	—	1	μA
I_{IL}	Input LOW current	$V_{CC} = \text{Max.}$, $V_i = 0\text{V}$		—	—	-1	μA
V_{IK}	Clamp diode voltage	$V_{CC} = \text{Min.}$, $I_N = -18\text{mA}$		—	-0.7	-1.2	V
I_{IOS}	Short-circuit current	$V_{CC} = \text{Max.}$, ⁽³⁾ $V_O = \text{GND}$		—	—	-35	mA
V_{OH}	Output HIGH voltage	$V_{CC} = \text{Min.}$, $V_{\text{IN}} = V_{\text{IL}}$	$I_{\text{OH}} = -20\mu\text{A}$	4.4	4.499	—	V
			$I_{\text{OH}} = -4\text{mA}$	3.84	4.3	—	V
V_{OL}	Output LOW voltage	$V_{CC} = \text{Min.}$, $V_{\text{IN}} = V_{\text{IH}}$	$I_{\text{OL}} = 20\mu\text{A}$	—	.001	0.1	V
			$I_{\text{OL}} = 4\text{mA}$	—	0.17	0.33	V
I_{CC}	Quiescent power supply current	$V_{CC} = \text{Max.}$, $V_{\text{IN}} = \text{GND}$ or V_{CC} , $I_O = 0$		—	2	10	μA

Overview: Digital Circuits

- * Logic Signals
- * Logic Families
- * IC Fabrication
- * CMOS Logic

→ Self-study topic (*)




Chapters 1 & 3 – “Digital Design: Principles and Practices” book

(*) This is complemented by a video shown in class.

ICs: back to basics

 - **Integrated Circuits** (ICs) are made of silicon, which in turn is created from sand. However, the manufacturing process of ICs is extremely complex and expensive.



Silicon and ICs


- **Silicon** is a semiconductor. This means that it can be altered to act as either a conductor, allowing electricity to flow, or as an insulator preventing the flow of electricity.
- **Silicon chips:**
 - have a surface area of similar dimensions to a thumb nail (or even smaller);
 - are 3-dimensional structures composed of microscopically thin layers (perhaps as many as 20) of insulating and conducting material on top of the silicon.

Silicon Ingots: Definition

- Semiconductor devices are produced from *silicon ingots*.
- **Silicon ingots** is the name given to *silicon* in a single crystal form.
- **Ingots** are produced in a number of ways, but essentially, *high purity silicon* is melted down and then formed into **cylindrical rods** as shown below.



 Silicon ingots are made to the customer's specifications (usual diameter ~15-20cm).



Wafers *versus* Silicon Ingots



- **Rods** (or *silicon ingots*) are sliced into very thin *wafers*, using special diamond cutting technology.
- **Wafers**:
 - are treated (i.e., polished and chemically treated) to remove any roughness and/or damage;
 - are very thin (usually only *0.06mm* in width).
- **ICs** are built from the *wafers*.

Silicon ingot and the *wafers* that are cut from the ingot.



Creating ICs on Wafers

  - **Wafers** are divided up so that many chips can be printed on them.



Finished wafers.

- How are all connectors, resistors, transistors and capacitors added to the wafer to make up an IC?
 - New (very thin) **layers** are added to the original wafer.
 - Each additional layer defines more and more of the completed IC.

The Die

- **Wafers** *versus* **chips**: One wafer can yield hundreds of finished chips, that are cut individually using a diamond saw.
- **Die**: The industry term for individual chips.
- **Die size** varies depending on the chip:
 - The larger the individual chip's die size, the greater the waste of silicon area when a fault arises on a chip.
 - **Example**: If a wafer is divided to make 40 chips and 10 random faults occur, then there'll be a wastage of 25%.
But if the wafer is divided to make 200 chips and 10 random faults occur, then wastage will be only 5%.

Wafer Yield

- **Yield of the wafer:** The percentage of functioning chips.
- Yields vary substantially depending on:
 - complexity of the device being produced;
 - feature size used.
- **Acceptable yield values:**
 - any yield value of 50% is reported;
 - yield values of 80% to 90% are regarded as very good.



Producing good yield values is important, since **a single short circuit**, caused by two wires touching in a 30+ million transistor chip, **is enough to cause chip failure!**

Feature Size


- **Feature Size:** Refers to the size of a transistor or to the width of the wires connecting transistors on the chip. *Examples:*
 - One micron (i.e., 1/1000 of a millimetre) *used to be* a common feature size.
 - State of the art chips are now using sub-micron feature sizes between 0.25 (in 1997) to 0.13 (in 2001) (i.e., between 250 and 130 nanometres).



The smaller the feature size, the more transistors there are available on a given chip area.

A million nanometers

 The pinhead sized patch of this thumb is a million nanometers across.



Smaller Feature Size (1/2)

- **Advantages:**

- A greater number of transistors per die means a smaller die size, and this means more chips per wafer.
- A microprocessor using a smaller feature size than its predecessor will be smaller, run faster and use less power.
- Since more of these smaller chips can be obtained from a single wafer, each chip will cost less (this is one of the reasons for cheaper processor chips).
- A reduced feature size makes it possible to build more complex microprocessors, e.g., the Pentium III which uses around 30 million transistors.

Smaller Feature Size (2/2)

- **Disadvantages:**
 - A reduced feature size means an **increase in the density of transistors per chip area**, and this has led to power consumption and power dissipation problems.
 - **Example:**
 - **CPUs** typically dissipate about the same heat per square inch as an electric cooker generates (and **sometimes require cooling fans or water cooling systems**).

Overview: Digital Circuits

- * Logic Signals
- * Logic Families
- * IC Fabrication
- * CMOS Logic




Chapters 1 & 3 – “Digital Design: Principles and Practices” book

CMOS Logic

- As seen before:
 - The **building blocks** in CMOS are MOS transistors.
 - CMOS operates from a 5 volts power supply (*usually!*).
- The **Voltage-logic connection** is interpreted as follows:

 
Typical **Logic levels**
for CMOS logic circuits.



MOS Transistors

- **MOS transistor**: a 3-terminal device.
 - The voltage applied to one terminal controls the resistance between the remaining two terminals.
 - The **three terminals** are:

- *Gate*;
- *Source*;
- *Drain*.

 


The *names* refer to the type of *semiconductor material* used for the resistance-controlled terminals.

- **Types of MOS transistors**:
 - *n-channel*
 - *p-channel*


N-Channel MOS (NMOS) Transistor

- **Drain** on NMOS: usually is at a *higher* voltage than the **source**.
- **Notation:**
 - V_{gs} = voltage from **gate** to **source**
 - R_{ds} = resistance from **drain** to **source**
- **How it works:**
 - $V_{gs} \geq 0$ (usually).
 - If $V_{gs} = 0$, then R_{ds} will be very high (so, *no output*).
 - If voltage on the **gate** is increased (i.e., increase on V_{gs}), then R_{ds} decreases (so, *there is an output*).

 

P-Channel MOS (PMOS) Transistor

- **PMOS** operation similar to **NMOS**, but **drain** is usually at a *lower* voltage than the **source**.
- **Notation:**
 - V_{gs} = voltage from **source** to **gate**
 - R_{ds} = resistance from **source** to **drain**
- **How it works:**
 - $V_{gs} \leq 0$ (usually).
 - If $V_{gs} = 0$, then R_{ds} will be very high (so, *no output*).
 - If voltage on the **gate** is decreased (i.e., decrease on V_{gs}), then R_{ds} decreases (so, *there is an output*).

 



CMOS Inverter

- **CMOS inverter circuit:** the simplest CMOS circuit, requires only one each of a PMOS and an NMOS.

- **Functional behaviour:**

V_{IN}	Q1	Q2	V_{OUT}
0V (L)	off	on	5V
5V (H)	on	off	0V


- **Logic symbol:**

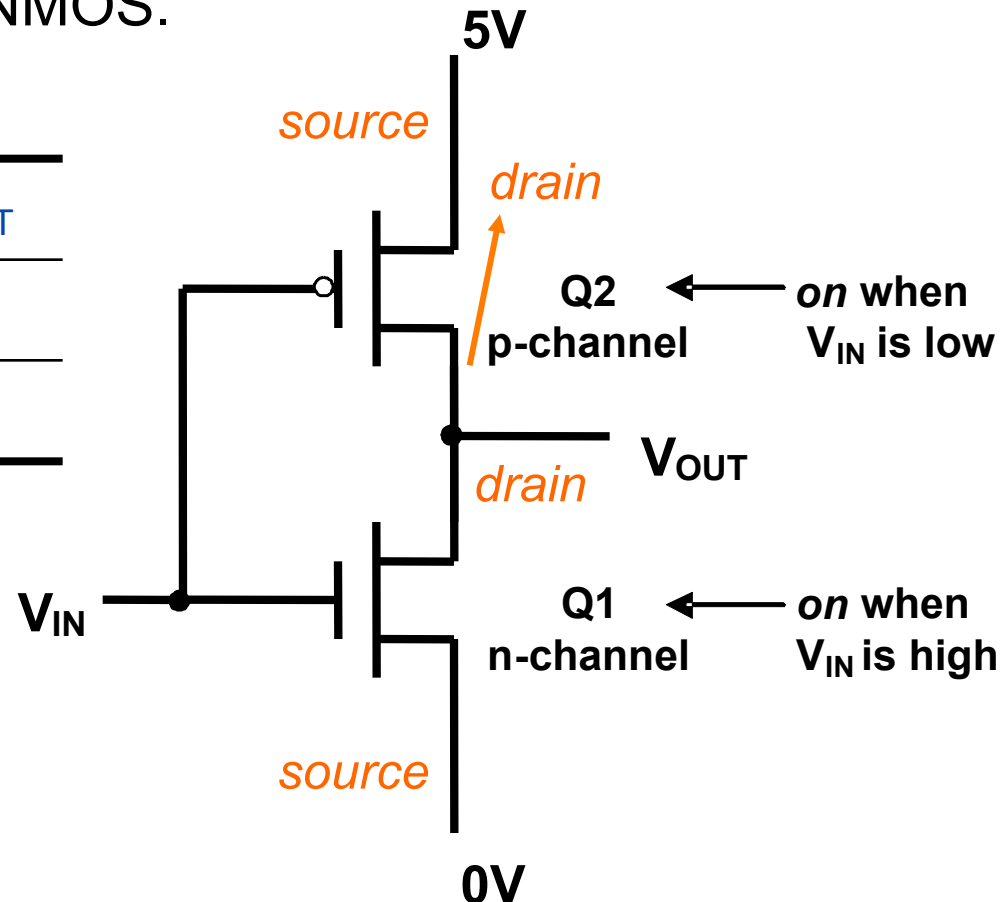 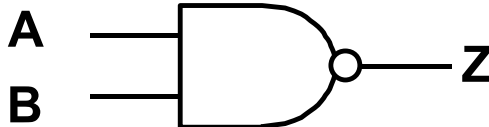


CMOS 2-Input NAND

- **CMOS NAND circuit:** a k -input gate uses both k PMOS and k NMOS transistors.
- **Functional behaviour:**

A	B	Q1	Q2	Q3	Q4	Z
L	L	off	on	off	on	H
L	H	off	on	on	off	H
H	L	on	off	off	on	H
H	H	on	off	on	off	L

- **Logic symbol:** 

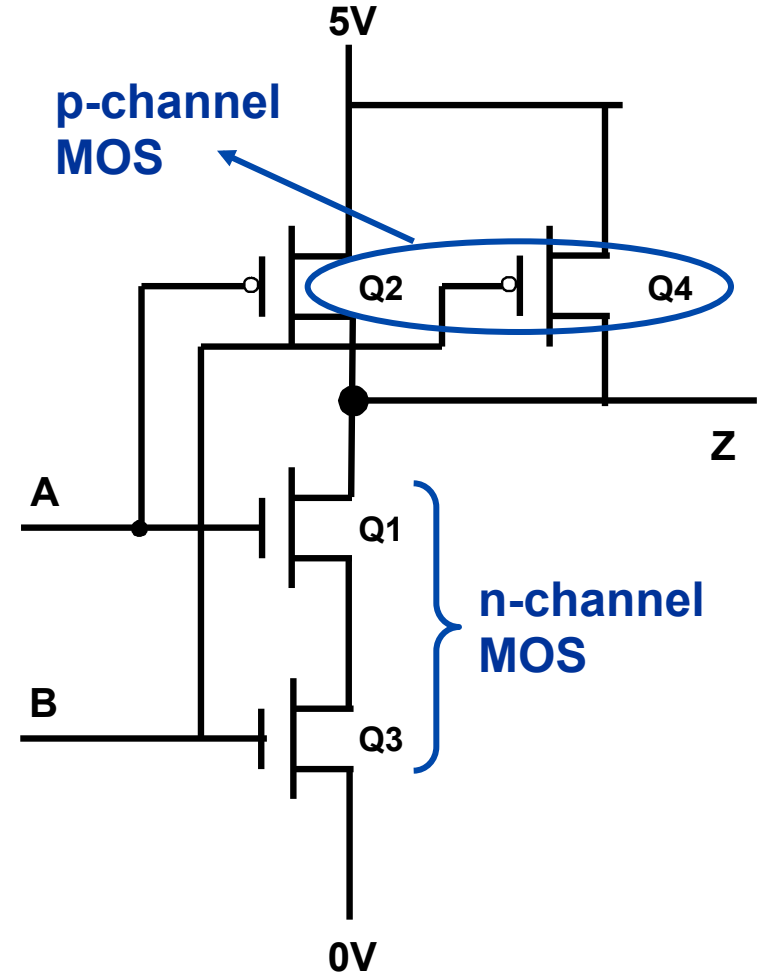



CMOS 2-Input NOR

- **CMOS NOR circuit:** a k -input gate uses both k PMOS and k NMOS transistors.

- **Functional behaviour:**

A	B	Q1	Q2	Q3	Q4	Z
L	L	off	on	off	on	H
L	H	off	on	on	off	L
H	L	on	off	off	on	L
H	H	on	off	on	off	L

- **Logic symbol:**

  

CMOS Electrical Properties

- The **electrical behaviour of a CMOS gate** can be characterised by its *electrical properties*. They include, apart from *logic voltage levels*:
 - *Noise margins* → How much noise it takes to corrupt a worst-case output voltage into a value that can not be recognised by an input.
 - *Fan-out* → Number of inputs that the gate can drive/feed without exceeding its worst-case specifications.
 - *Speed (propagation delay)* → Time necessary for a change in the input signal to result in a change to the output signal.
 - *Power consumption* → Most CMOS circuits have low *static power dissipation*.



Dilemma faced in electronic design – increasing the *speed* (i.e., decreasing the *propagation delay*) typically results in higher *power dissipation*, and vice versa.