


Timing Hazards and Output Glitches (1/3)

- **Output glitch**: A momentary unexpected output change (short pulse) when an input changes; usually caused by gate propagation delays.
- **Hazards**: A timing hazard exists in a combinational circuit when it produces an output glitch when one or more inputs change.
 - **Static Hazards** (*static-1* and *static-0*): when 1 input variable changes, the output changes momentarily before stabilising on the correct value.
 - Can usually be fixed by adding redundant logic (*Consensus Theorem – T11*).
 - **Dynamic Hazards**: possibility of an output changing more than once as a result of a single input change.


Timing Hazards and Output Glitches (2/3)

- Example of *static-1 hazard*:

		BC			
A	BC	00	01	11	10
		0	0	1	0
0	0	0	0	1	0
1	1	1	1	1	0

 


1-hazard

 

Timing Hazards and Output Glitches (3/3)

- Example of *static-1 hazard* (cont.):

 

A \ BC				
	00	01	11	10
0	0	0	1	0
1	1	1	1	0

removing the
static-1 hazard

$$F = AB' + BC + AC$$

