

Q1



- Using a 5-variable Karnaugh Map, **find the minimal PoS** for the Switching Algebra function,

$$G(M, N, O, P, Q) = \sum m(1, 2, 5, 8, 11, 12, 16, 20, 21, 22, 24) + d(0, 4, 6, 28, 31)$$

M = 0

		PQ			
		00	01	11	10
NO	00				
	01				
	11				
	10				

M = 1

		PQ			
		00	01	11	10
NO	00				
	01				
	11				
	10				



- A small company has **100 shares of stock**, and each share entitles its owner to 1 vote at a stockholders' meeting.
- There are only **4 shareholders**: Mr Adams owns 10 shares, Mrs Brown owns 20 shares, Ms Cayman owns 30 shares and Mr Davidson owns 40 shares. A two-thirds majority is required in order to pass a measure at a stockholders' meeting.
- An important and sensitive vote is coming up and it has been decided that a degree of secrecy is necessary. This is to be achieved by providing each stockholder with a switch that can be switched one way for “yes” and another way for “no”. ***A switching circuit is to be designed to turn on a light if the vote achieves the required two-thirds majority.***
- Assume that the switch provide logic **1** for “yes” and logic **0** for “no”.
 - Identify those **combinations of shareholders that hold between them two-thirds or more of the shares**, and write the **Boolean expression that describes the required behaviour of the switching circuit**. Then derive the **simplest Boolean expression for this circuit in the form of a PoS**, using a Karnaugh map.
 - Your answer must also include clearly the variables and their meaning (i.e. inputs and output) of your resulting switching circuit.

Let us denote the following Boolean variables:

A – vote from Mr Adams (A = 1 is a “yes” vote; A = 0 is a “no” vote)

B – vote from Mrs Brown (B = 1 is a “yes” vote; B = 0 is a “no” vote)

C – vote from Ms Cayman (C = 1 is a “yes” vote; C = 0 is a “no” vote)

D – vote from Mr Davidson (D = 1 is a “yes” vote; D = 0 is a “no” vote)

The combinations of shareholders that lead to a majority of at least two-thirds (i.e., > 66.7%) are:

CD (70% majority); ABD (70% majority); ACD (80% majority); BCD (90% majority); ABCD (100% majority).

(Mr Adams owns 10 shares, Mrs Brown owns 20 shares, Ms Cayman owns 30 shares and Mr Davidson owns 40 shares)

- Therefore, the required logic function is:

$$F(A,B,C,D) = CD + ABD + ACD + BCD + ABCD$$

A	B	C	D	F
0	0	0	0	
0	0	0	1	
0	0	1	0	
0	0	1	1	
0	1	0	0	
0	1	0	1	
0	1	1	0	
0	1	1	1	
1	0	0	0	
1	0	0	1	
1	0	1	0	
1	0	1	1	
1	1	0	0	
1	1	0	1	
1	1	1	0	
1	1	1	1	

AB \ CD	CD			
	00	01	11	10
00				
01				
11				
10				

MPS of F:

Q3


- **Problem:** Suppose an alarm is to sound if the key is in the ignition and the door is open, **or** if the key is out of the ignition and the brake is off, **or** if the door is open and the brake is off. At all other times, the alarm must be silent.
- Derive a logic equation for the alarm going off.

Q4

A binary-to-hexadecimal code converter will be designed. Given a 4-bit binary input WXYZ, the code converter generates the 7-bit output necessary to display the hex characters '0', '1', '2', '3', '4', '5', '6', '7', '8', '9', 'A', 'b', 'C', 'd', 'E' and 'F' as follows:



Figure below shows the naming of each LEDs in a 7- segments display:

 

- Produce a truth table for the segment 'a' in the 7-segments display.
- Use a Karnaugh map to find a minimal sum of products for output "a".

Q5

A washing machine alarm tone (**Z**) is designed so that it accepts 3 input signal lines. Line **A** is from the machine door control, whereas lines **B** and **C** are from the wash cycles or states control unit. The following two conditions apply:

- The “door of the washing machine is closed” is represented by **A=1**, otherwise **A=0**.
- The remaining 2 inputs (**B** and **C**) decide the position or the state of the wash (i.e., there are 4 different wash cycles numbered **0-3**, equivalent to **00**, ..., **11**).

1) Write the Truth Table for the washing machine alarm tone (**Z**) that produces a *logic 1* (i.e., it rings the alarm bell) when the washing machine has the door closed and the wash cycle is in one of the following states: state **0**, state **1** or state **3**.

2) Write the *minterm expansion* for **Z** and simplify algebraically to a minimum *Sum of Products* form. Show all your work.

- 3) Draw a clearly labelled circuit logic diagram for the minimised equation.
- 4) Rewrite the simplified design obtained in *part ii)* as a NAND gate implementation. How many logic gates are now necessary to implement this circuit design?

Q6

Consider the following problem description: “Design a combinational circuit that detects number **1** and prime numbers in the range **0-7**, based on the combined value of its inputs.”

Answer the following questions with reference to the problem description above:

- 1) Write the Truth Table for this circuit, indicating clearly all its inputs and output.
- 2) Derive a Switching Algebra expression for the circuit, based on the Truth Table obtained in *part 1*), and then simplify it using appropriate Switching Algebra theorems.
- 3) Draw a clearly labelled circuit logic diagram for the minimised equation.

Q7

Consider the combinational circuit described by the Switching Algebra expression:

$$F(A,B,C,D) = ABC' + ACD' + AB'D + BC'D.$$

- 1) Expand the expression above into a *canonical Sum of minterms*.
- 2) Simplify the expression above using a *Karnaugh Map* and give your answer in the form of a *minimal Product of Sums*, showing all your work.