

Revision

- * Introduction
- * Bistable Elements
- * Latches & Flip-Flops
- * Analysis Procedure
- * Design Procedure



Chapter 7 – “Digital Design: Principles and Practices” book




Learning Objectives for the Session

By the end of the session all students will be able to:

- 1) recognise the different types of latches and flip-flops, introduced in this module.
- 2) explain the differences and similarities between these different latches and flip-flops.
- 3) analyse different types of latch and flip-flop to understand how a change on the input will affect the outputs.

Latches

- SR latch – Simplest type.

   

Latches and Flip-Flops




- SR latch – Simplest type.

<i>Inputs</i>		<i>Outputs</i>	
S	R	Q	QN
0	0	last Q	last QN
0	1	0	1
1	0	1	0
1	1	0	0

Illegal (invalid)
operation when both
inputs are *True*.

Latches

   - SR latch with control line – Same as SR but AND gate connected to each input. The same control signal is applied one input of each AND gate. Other input is S or R, respectively.



Latches




- SR latch with control line – Same as SR but AND gate connected to each input. The same control signal is applied one input of each AND gate. Other input is S or R, respectively.

<i>Inputs</i>			<i>Outputs</i>	
S	R	C	Q	QN
0	0	1	last Q	last QN
0	1	1	0	1
1	0	1	1	0
1	1	1	0	0
x	x	0	last Q	last QN

*Same as
RS latch*

Latches

   - D(-type) latch – Same as SR but has only 1 input D (equivalent to S). $R = D' \equiv S'$. Solves problem of $S = R = 1$ being presented to latch which caused it to give an illegal output, namely: $Q = Q' = 0$



Latches

- D(-type) latch – Same as SR but has only 1 input D (equivalent to S). $R = D' \equiv S'$. Solves problem of $S = R = 1$ being presented to latch which caused it to give an illegal output, namely: $Q = Q' = 0$

<i>Inputs</i>		<i>Outputs</i>	
C	D	Q	QN
1	0	0	1
1	1	1	0
0	x	last Q	last QN

reset state

set state

Latches

S	R	Q	QN
0	0	last Q	last QN
0	1	0	1
1	0	1	0
1	1	0	0

RS latch

S	R	C	Q	QN
0	0	1	last Q	last QN
0	1	1	0	1
1	0	1	1	0
1	1	1	0	0
x	x	0	last Q	last QN

RS latch with control

*Same as
RS latch*

C	D	Q	QN
1	0	0	1
1	1	1	0
0	x	last Q	last QN

D latch

Latches

Latch stores last state

S	R	Q	QN
0	0	last Q	last QN
0	1	0	1
1	0	1	0
1	1	0	0

RS latch

S	R	C	Q	QN
0	0	1	last Q	last QN
0	1	1	0	1
1	0	1	1	0
1	1	1	0	0
x	x	0	last Q	last QN


RS latch with control

C	D	Q	QN
1	0	0	1
1	1	1	0
0	x	last Q	last QN

D latch

Latches

 - The circuit symbol of a latch is a rectangular box with 2 outputs, Q and Q' and 1 or more inputs.




Difference between Latch and Flip-Flop

- Difference between latch and flip-flop – **Latch** has no clock input so its operation is **not synchronized** with the clock. **Flip-flop** has a clock input so its operation **is synchronized** with the clock
- Only flip-flop is suitable for use in a synchronous sequential circuit

Clock Signal

 
- Image below shows a typical clock signal



$$\text{frequency} = 1/t_{\text{per}}$$

Clock Signal

 
- In the circuit symbol for a flip-flop we use a triangle and the letters CLK to denote that the flip-flop is triggered on a clock edge.



- An edge triggered flip-flop will ignore the inputs while the clock pulse is at a constant level. It will only set the outputs on clock pulse transitions.

Clock Signal

 
- There are 2 edges associated with the clock.



- Could trigger flip-flop from either the rising or falling edge of the clock.

Clock Signal

 
- There are 2 edges associated with the clock.



- Could trigger flip-flop from either the rising or falling edge of the clock.


Flip-Flops

 - The SR flip-flop – Same as SR latch with control line but the control line attached to a clock signal.






Flip-Flops

 - The D flip-flop – Same as D latch but includes a clock input



   
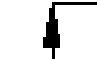


Flip-Flops

- A JK flip-flop – Same as SR flip-flop but additional AND gates are added before the S and R inputs. One inputs to AND gate on S is connected to Q' . One inputs to AND gate on R is connected to Q



Flip-Flops





- A JK flip-flop – Normally edge triggered.

J	K	CLK	Q	QN
x	x	0	last Q	last QN
x	x	1	last Q	last QN
0	0		last Q	last QN
0	1		0	1
1	0		1	0
1	1		last QN	last Q

*Flip-flop
stores last
state*

Flip-Flops

- A JK flip-flop – Normally edge triggered.


J	K	CLK	Q	QN
x	x	0	last Q	last QN
x	x	1	last Q	last QN
0	0		last Q	last QN
0	1		0	1
1	0		1	0
1	1		last QN	last Q

*Same as
RS latch*

- Notice that, unlike for the RS flop-flop, there is no illegal state. Due to the feedback from output to input S and R are always different


Flip-Flops

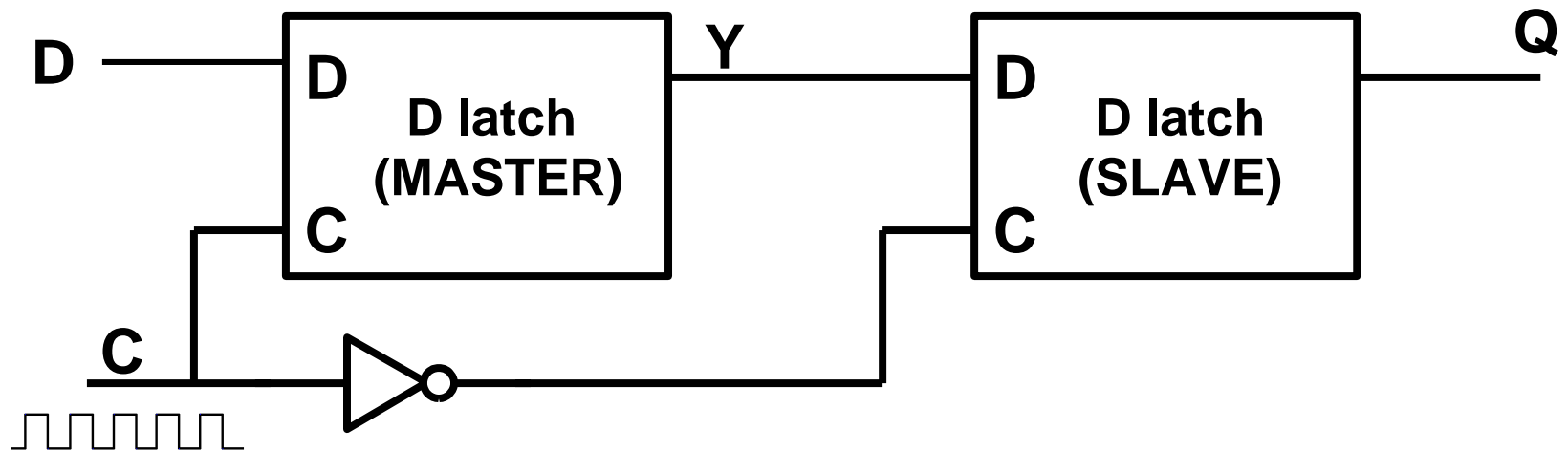- Master Slave – The name for a way of ganging together flip-flop. Output of Master flip-flop is connected to input of Slave flip-flop. Clock input to Slave is inverted with respect to that of Master.
- Figure below shows Master Slave connection of D flip-flops




Flip-Flops

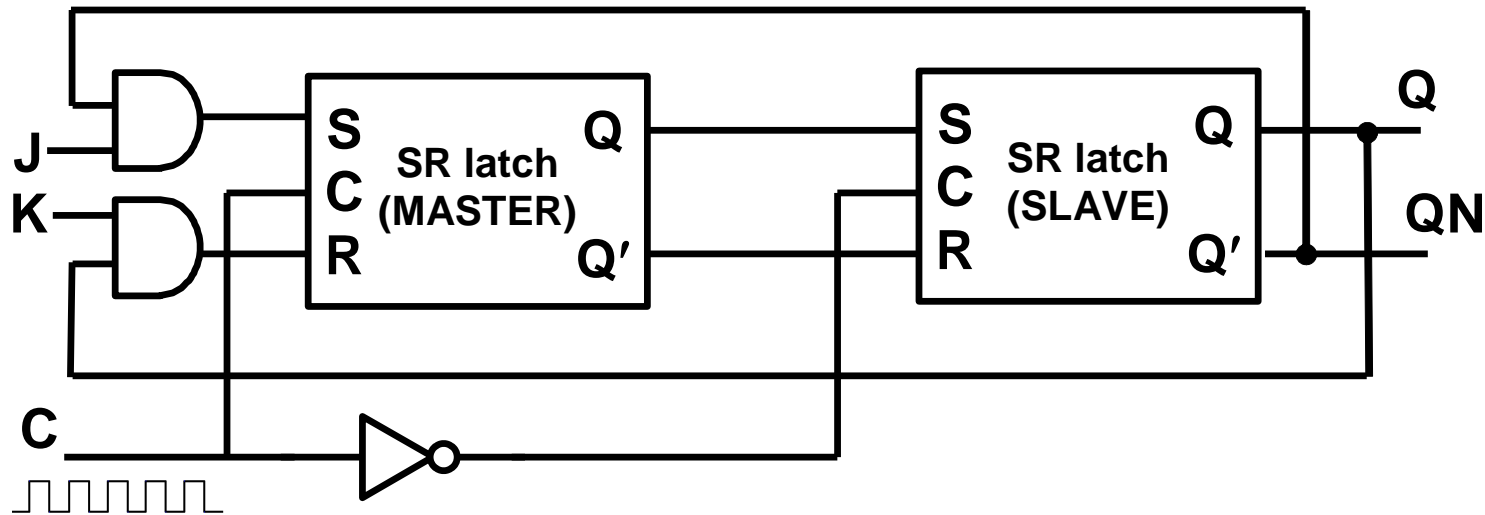- Figure below shows Master Slave connection of JK flip-flops




Flip-Flops

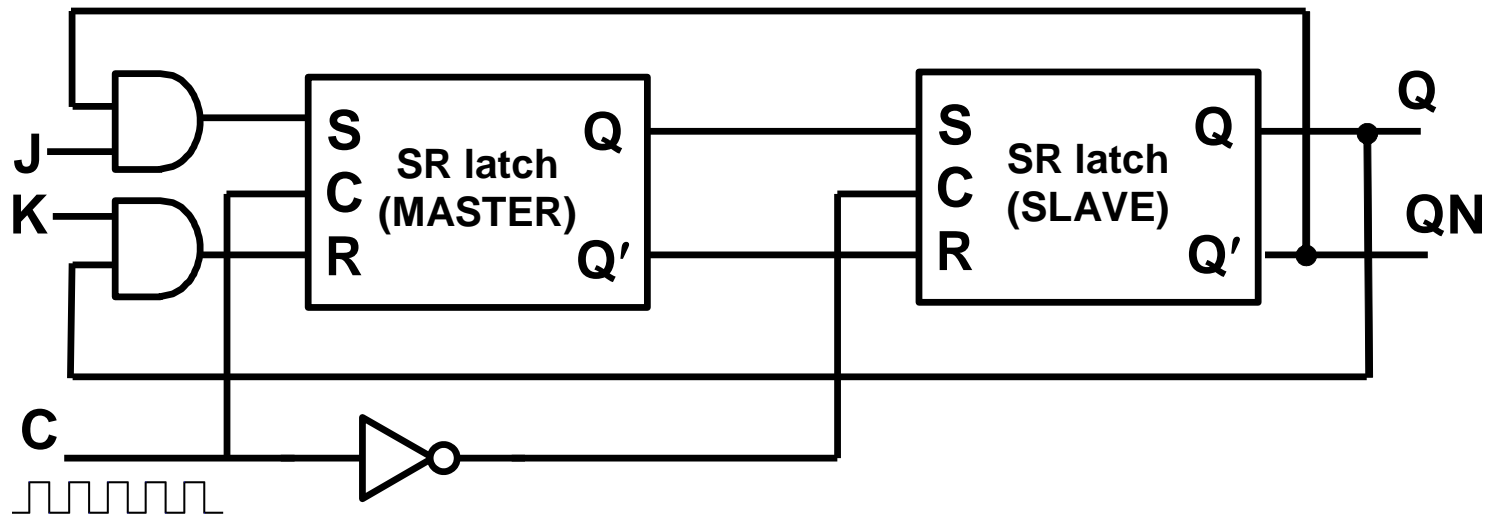- Figure below shows Master Slave connection of JK flip-flops



Analysis of Flip-Flop Operation

 - Figure below shows an SR latch. Assume that we find it in this initial condition



OR gate
Truth table →


Input		Output
A	B	F
0	0	0
0	1	1
1	0	1
1	1	1

S	R	Q	QN
0	0	last Q	last QN
0	1	0	1
1	0	1	0
1	1	0	0

RS latch

Analysis of Flip-Flop Operation

 - Figure below shows an SR latch. Assume that we now raise S high (i.e. $S = 1$)



OR gate
Truth table →


Input		Output
A	B	F
0	0	0
0	1	1
1	0	1
1	1	1

S	R	Q	QN
0	0	last Q	last QN
0	1	0	1
1	0	1	0
1	1	0	0

RS latch

Analysis of Flip-Flop Operation

 - Figure below shows an SR latch. Assume that we now raise S high (i.e. $S = 1$)



t_{delay} = Propagation delay through gate

OR gate
Truth table →


Input		Output
A	B	F
0	0	0
0	1	1
1	0	1
1	1	1

S	R	Q	QN
0	0	last Q	last QN
0	1	0	1
1	0	1	0
1	1	0	0

RS latch

Analysis of Flip-Flop Operation

 - Figure below shows an SR latch. Assume that we now raise S high (i.e. $S = 1$)



OR gate
Truth table \rightarrow


Input		Output
A	B	F
0	0	0
0	1	1
1	0	1
1	1	1

S	R	Q	QN
0	0	last Q	last QN
0	1	0	1
1	0	1	0
1	1	0	0

RS latch

Analysis of Flip-Flop Operation

 - Figure below shows an SR latch. Now assume that we set S low (i.e. $S = 0$) and set R high (i.e. $R = 1$) in that order.



OR gate
Truth table →


Input		Output
A	B	F
0	0	0
0	1	1
1	0	1
1	1	1

S	R	Q	QN
0	0	last Q	last QN
0	1	0	1
1	0	1	0
1	1	0	0

RS latch

Analysis of Flip-Flop Operation

 - Figure below shows an SR latch. Now assume that we set S low (i.e. $S = 0$) and set R high (i.e. $R = 1$) in that order.



OR gate
Truth table →


Input		Output
A	B	F
0	0	0
0	1	1
1	0	1
1	1	1

S	R	Q	QN
0	0	last Q	last QN
0	1	0	1
1	0	1	0
1	1	0	0

RS latch

Analysis of Flip-Flop Operation

 - Figure below shows an SR latch. Now assume that we set S low (i.e. $S = 0$) and set R high (i.e. $R = 1$) in that order.



OR gate
Truth table →


Input		Output
A	B	F
0	0	0
0	1	1
1	0	1
1	1	1

S	R	Q	QN
0	0	last Q	last QN
0	1	0	1
1	0	1	0
1	1	0	0

RS latch

Analysis of Flip-Flop Operation

 - Figure below shows an SR latch. Now assume that we set S low (i.e. $S = 0$) and set R high (i.e. $R = 1$) in that order.



OR gate
Truth table \rightarrow


Input		Output
A	B	F
0	0	0
0	1	1
1	0	1
1	1	1

S	R	Q	QN
0	0	last Q	last QN
0	1	0	1
1	0	1	0
1	1	0	0

RS latch

Analysis of Flip-Flop Operation

 - Figure below shows an SR latch. Now assume that we set S low (i.e. $S = 0$) and set R high (i.e. $R = 1$) in that order.



OR gate
Truth table \rightarrow

Input		Output
A	B	F
0	0	0
0	1	1
1	0	1
1	1	1

S	R	Q	QN
0	0	last Q	last QN
0	1	0	1
1	0	1	0
1	1	0	0

RS latch

Learning Objectives for the Session

So hopefully you are now able to:

- 1) recognise the different types of latches and flip-flops, introduced in this module.
- 2) explain the differences and similarities between these different latches and flip-flops.
- 3) analyse different types of latch and flip-flop to understand how a change on the input will affect the outputs.