

### Solution to Q1:


Rewrite the indices of minterms in binary representation:

00001, 00010, 00101, 01000, 01011, 01100, 10000, 10100, 10101, 10110, 11000

Rewrite the indices of don't care terms in binary representation:

00000, 00100, 00110, 11100, 11111

Fill and circle the Karnaugh Map:

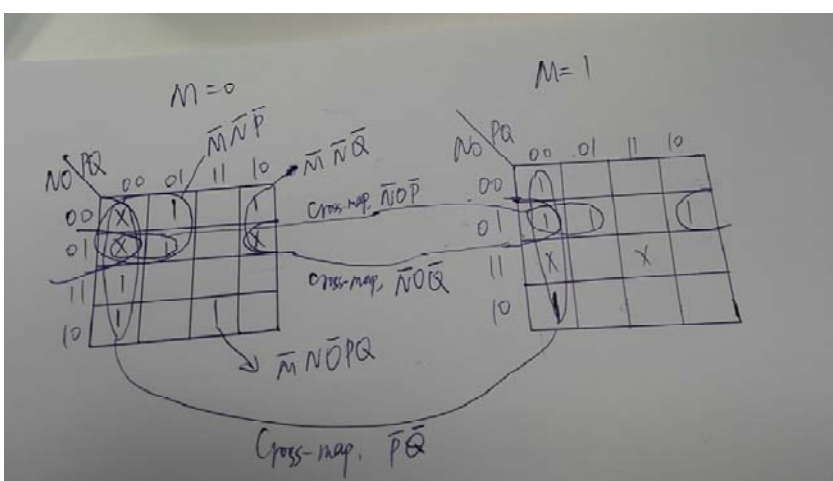


The minimal SOP is given by:

$$G(M, N, O, P, Q) = \bar{P}\bar{Q} + \bar{M}\bar{N}P + \bar{M}\bar{N}\bar{Q} + \bar{N}\bar{O}P + \bar{N}\bar{O}Q + \bar{M}\bar{N}\bar{O}PQ$$

I suggest to change the question to find the minimal SOP as the minimal POS is not covered by the slide


**Solution to Q2:**

The truth table is given by

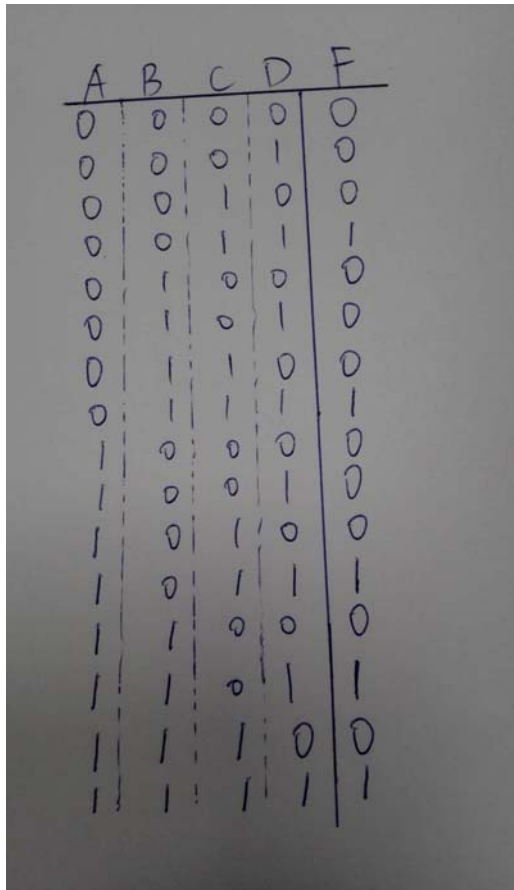

A	B	C	D	F
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

Fill and circle the Karnaugh Map as:

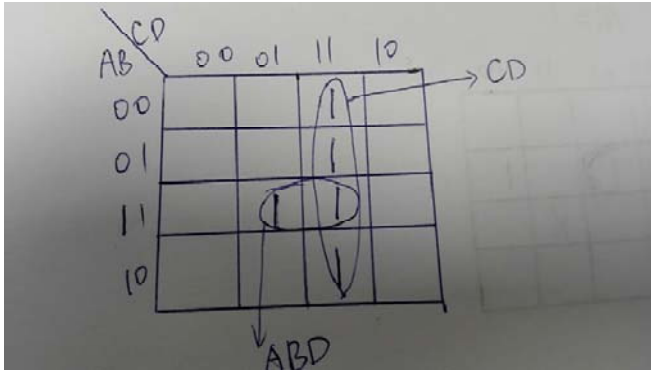

The MSP of F is given by:

$$F = ABD + CD$$

Again, change the question to find the MSP, rather than MPS.

**Solution to Q3:**

Let us denote the following Boolean variables:

- A- Status of the key (A=1: the key in ignition; A=0: otherwise.)
- B- Status of the door (B=1: the door is open; B=0, otherwise.)
- C- Status of the brake (C=1: the brake is on; C=0, otherwise.)
- D- Status of the alarm (D=1: the alarm is working; D=0, otherwise.)

The combinations of status that lead to the sounding of the alarm are given by:

$$AB, \bar{A}\bar{C}, B\bar{C}$$

The logic equation of the alarm sounding is given by:

$$F = AB + A'C' + BC'$$

Finally, the logic equation of the alarm going off is given by


$$F' = (AB + A'C' + BC')' = (A' + B')(A + C)(B' + C)$$

**Solution to Q4:**

The truth table for the segment 'a' is given by

W	X	Y	Z	a
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	0
1	1	0	0	1
1	1	0	1	0
1	1	1	0	1
1	1	1	1	1

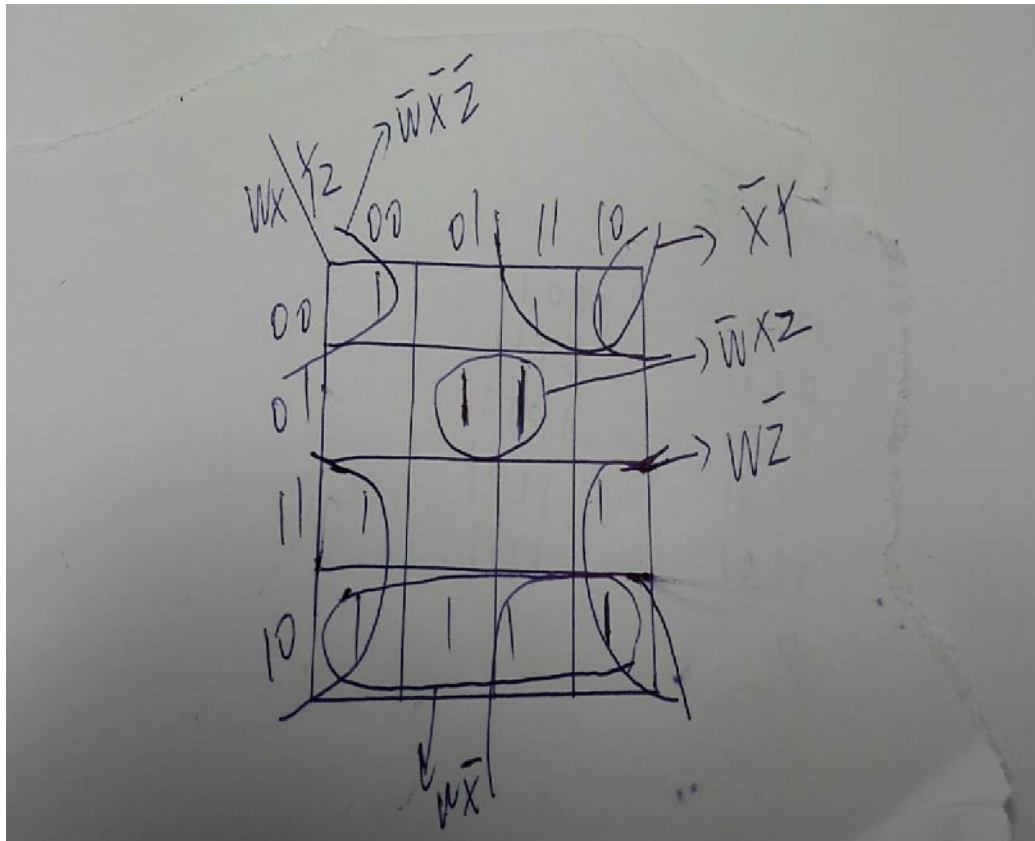Fill and circle the Karnaugh map as follows:



The minimal SOP is given by:

$$a = \bar{W}\bar{X}\bar{Z} + \bar{X}Y + \bar{W}XZ + WZ + W\bar{X}$$

**Solution to Q5:**

1) The truth table for Z is given by:

A	B	C	Z
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	1


2) The minterm expansion for Z is given by:

$$Z = A\bar{B}\bar{C} + A\bar{B}C + ABC$$

The minimum SOP is given by:

$$\begin{aligned} Z &= A(\bar{B}\bar{C} + \bar{B}C + BC) \\ &= A(\bar{B}\bar{C} + \bar{B}C + \bar{B}C + BC) \\ &= A(\bar{B}(\bar{C} + C) + C(\bar{B} + B)) \\ &= A(\bar{B} + C) \\ &= A\bar{B} + AC \end{aligned}$$

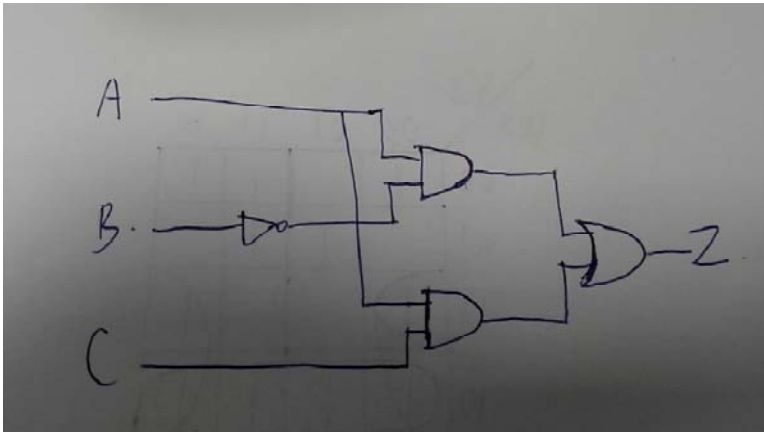3) The labelled circuit diagram is given by




4) Using De Morgan's theorem, we have

$$Z = (AB' + AC)''$$

$$= \left( (AB')' (AC)' \right)'$$

The circuit diagram is given by:



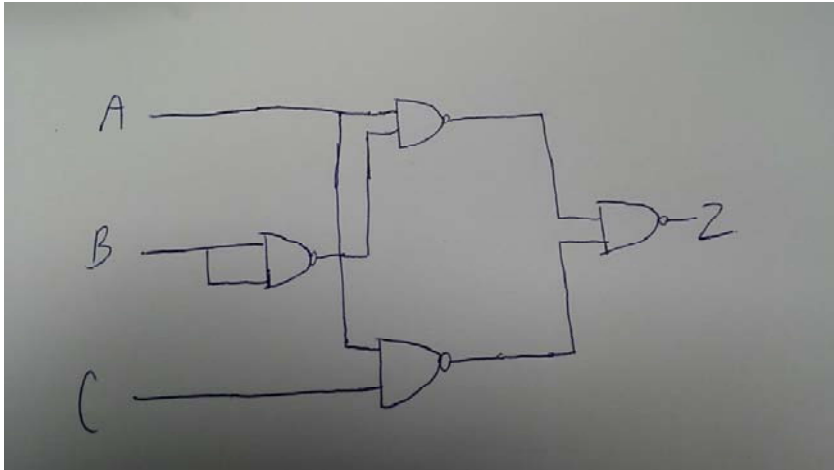

The number of logic gates required is four.

**Solution to Q6:**

- 1) Denote F as the detection indicator variable. It is equal to one when the input number is 1 or prime number. Denote A,B,C as the input binary expressions for the input number.

Then, the truth table is given by

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1


- 2) The Switching Algebra expression for the output F is given by

$$F = \bar{A}\bar{B}C + \bar{A}B\bar{C} + \bar{A}BC + A\bar{B}\bar{C} + ABC$$

It can be simplified as follows:

$$\begin{aligned} F &= \bar{A}\bar{B}C + \bar{A}B\bar{C} + \bar{A}BC + A\bar{B}\bar{C} + ABC \\ &= \bar{A}\bar{B}C + \bar{A}B\bar{C} + \bar{A}BC + \bar{A}BC + A\bar{B}\bar{C} + ABC \\ &= (\bar{A}\bar{B}C + \bar{A}BC) + (\bar{A}B\bar{C} + \bar{A}BC) + (A\bar{B}\bar{C} + ABC) \\ &= \bar{A}C(\bar{B} + B) + \bar{A}B(\bar{C} + C) + AC(\bar{B} + B) \\ &= \bar{A}C + \bar{A}B + AC \\ &= C(\bar{A} + A) + \bar{A}B \\ &= C + \bar{A}B \end{aligned}$$

- 3) The circuit is given by

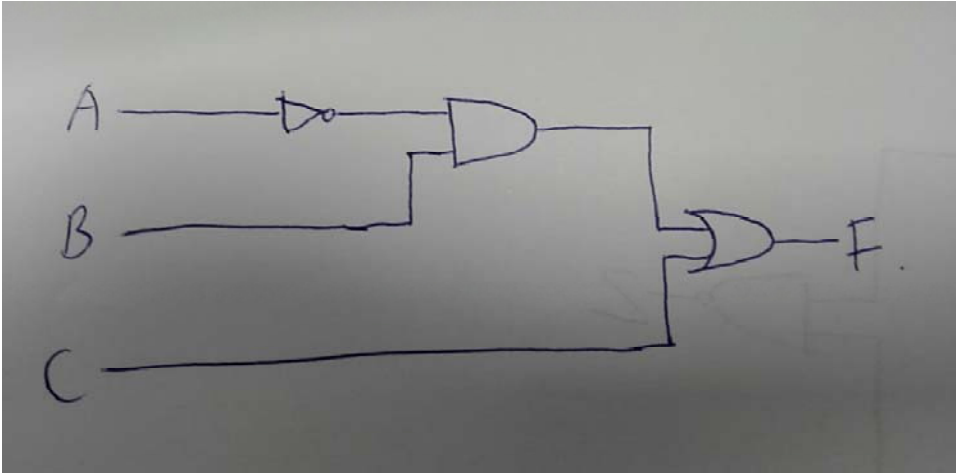


**Solution to Q7:**

- 1) The canonical sum of minterms can be obtained as follows:

$$\begin{aligned}
 F(A, B, C, D) &= ABC' + ACD' + AB'D + BC'D \\
 &= ABC'(D + D') + A(B + B')CD' + AB'(C + C')D + (A + A')BC'D \\
 &= ABC'D + ABC'D' + ABCD' + AB'CD' + AB'CD + AB'C'D + ABC'D + A'BC'D \\
 &= ABC'D + ABC'D' + ABCD' + AB'CD' + AB'CD + AB'C'D + A'BC'D
 \end{aligned}$$

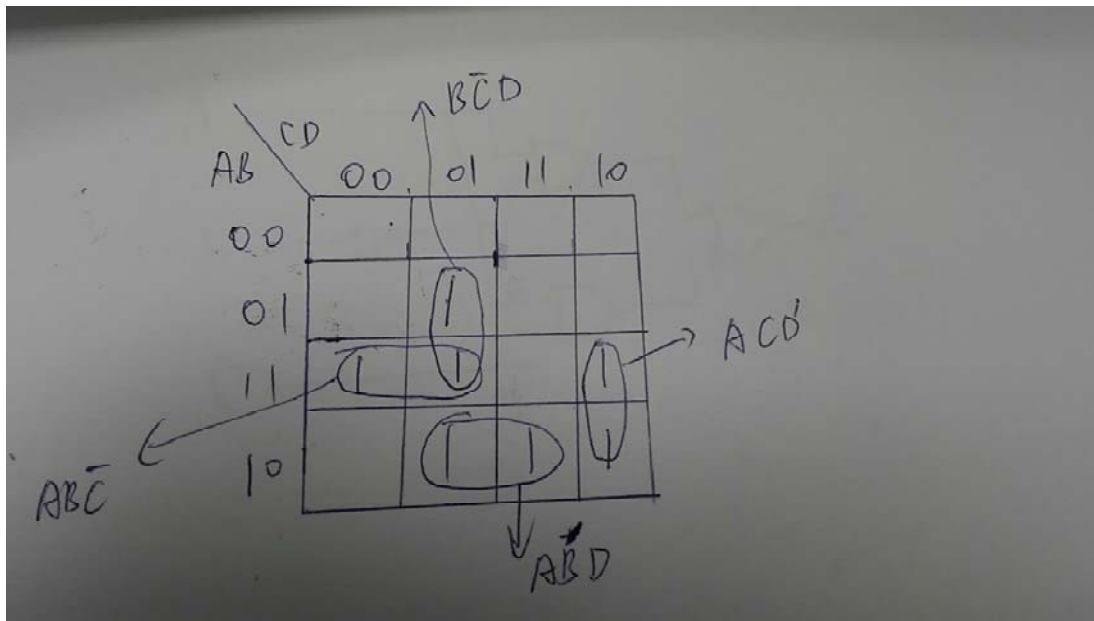- 2) Fill and circle the Karnaugh map as follows:



The minimal SOP is given by

$$F(A, B, C, D) = ABC' + BC'D + ACD' + AB'D$$

Again, the minimal POS is not covered in teaching slides. I suggest to use SOP.