 

Digital System Blocks


Buses

- Set of two or more electrical conductors representing a binary value




Buses

 - Often more than just a one-to-one connection



Buses

 - Often more than just a one-to-one connection




Selectors and Decoders

Selectors or *Multiplexers*

- Often labelled MUX
- 2-Input Selector:


S_0	Output
0	I_0
1	I_1

 

Selectors or *Multiplexers*

4-input Selector


S_1	S_0	Output
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3

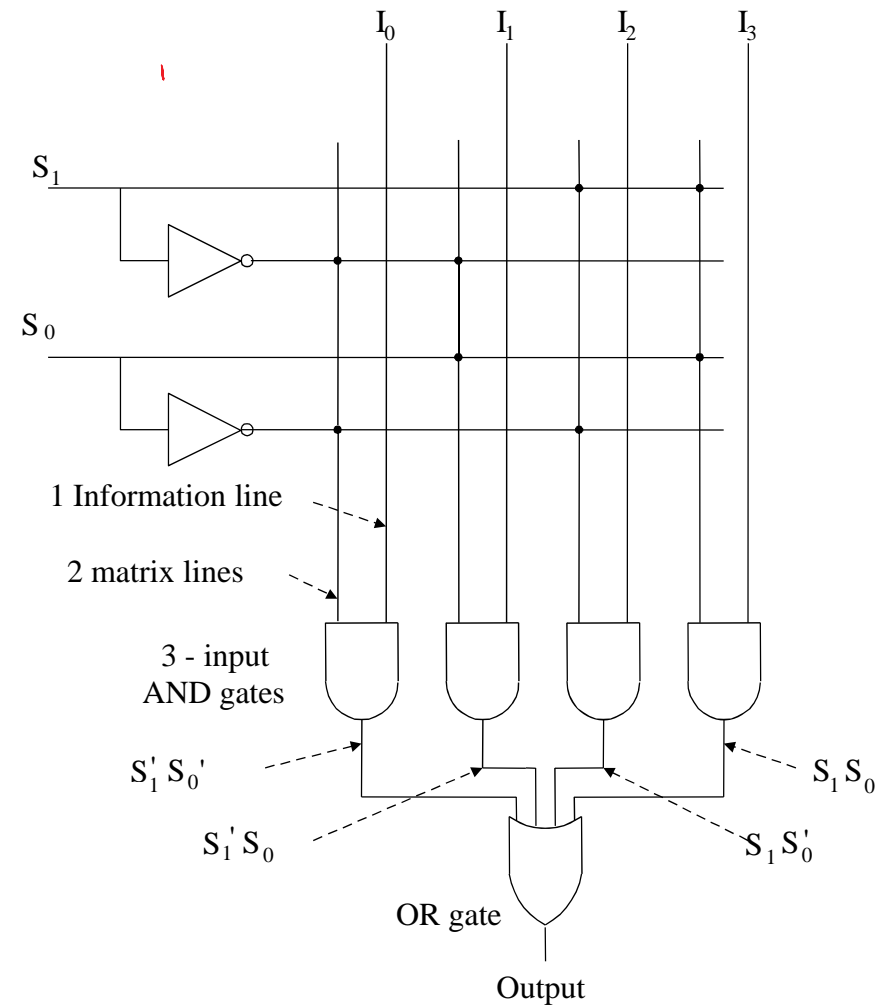

Multiplexers or Selectors


4-input Selector

S_1	S_0	Output
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3

 


Multiplexers or Selectors

2-Input 4-bit MUX

 


Multiplexers or Selectors

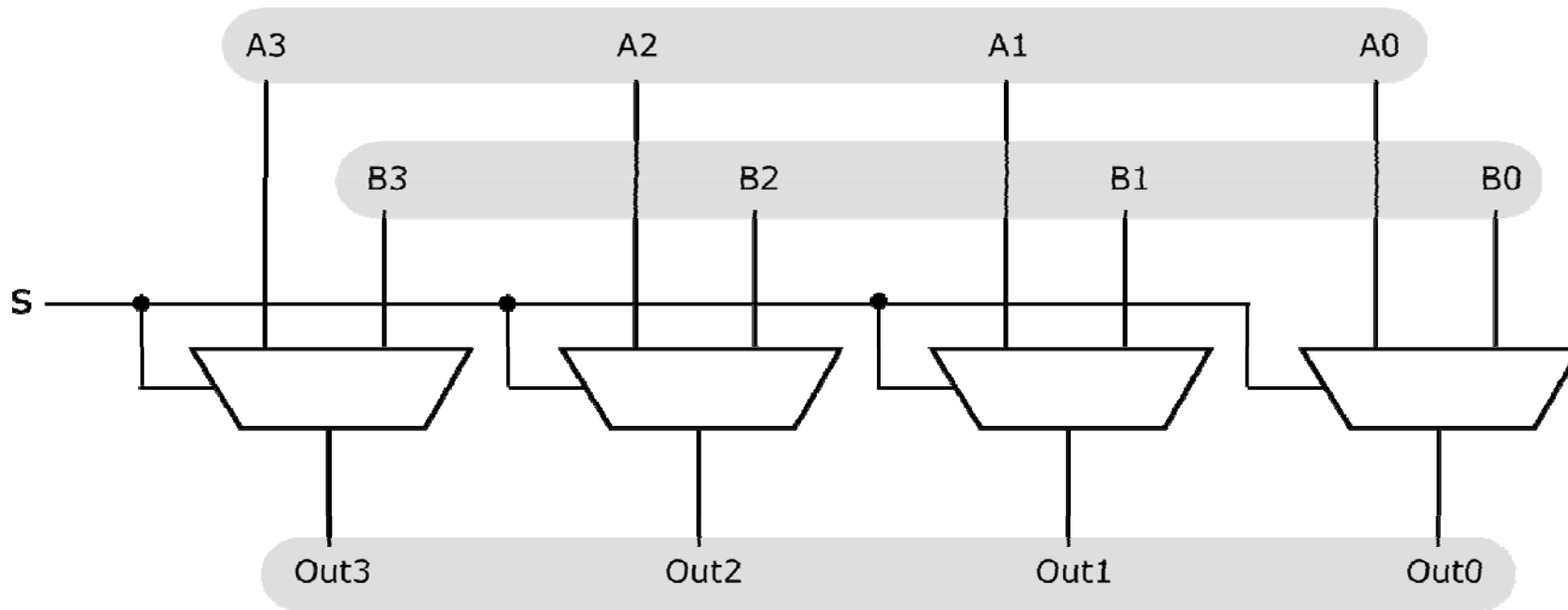
2-Input 4-bit MUX – Internal Implementation



Decoder or *Demultiplexer*

 

Magnitude Comparator (XNOR)

 

Basic comparator:


- output when $X = Y$
- complement gives $X \neq Y$

X	Y	Output
0	0	1
0	1	0
1	0	0
1	1	1

Other types give:

- $X > Y$
- $X < Y$
- complements give:
 - $X \leq Y$
 - $X \geq Y$

Multiple-bit magnitude comparator

 

For more than 1-bit comparisons, the XNORs are ANDed together

Exercise: Show that output of above 2-bit comparator is given by:

$$(A_0B_0 + A_0'B_0') \cdot (A_1B_1 + A_1'B_1')$$

Arithmetic Units

Adders - the half-adder

Half-adder:

- accepts two binary digit inputs (X & Y)
- produces Sum (S) & Carry (C) outputs

Arithmetically:

$$\begin{array}{r} X \\ Y \\ \hline C \quad S \end{array} +$$

Truth table:

X	Y	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0





		Y	
		0	1
X	0	0	1
	1	1	0
		Sum	

$$S = X\bar{Y} + \bar{X}Y = X \oplus Y$$

		Y	
		0	1
X	0	0	0
	1	0	1
		Carry	

$$C = XY$$

Examples of half-adder implementations

    


Exercise:

Show that for all circuits:

$$S = X\bar{Y} + \bar{X}Y$$

$$C = X \cdot Y$$


Half-adder NAND gate implementation

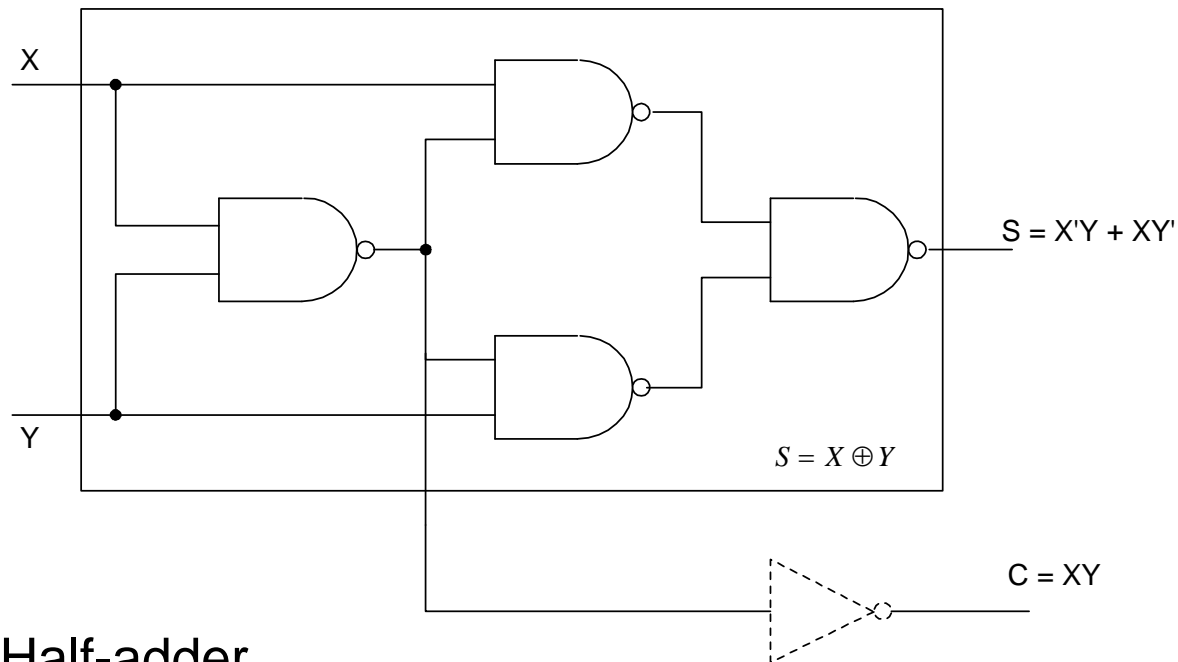


Half-adder

- Arithmetic $X + Y$
- Max gate delay 3 units
 - Sum* has 3 units delay
 - Carry* has 2 units delay (*Carry'* has 1 unit delay)

Effect of Delay

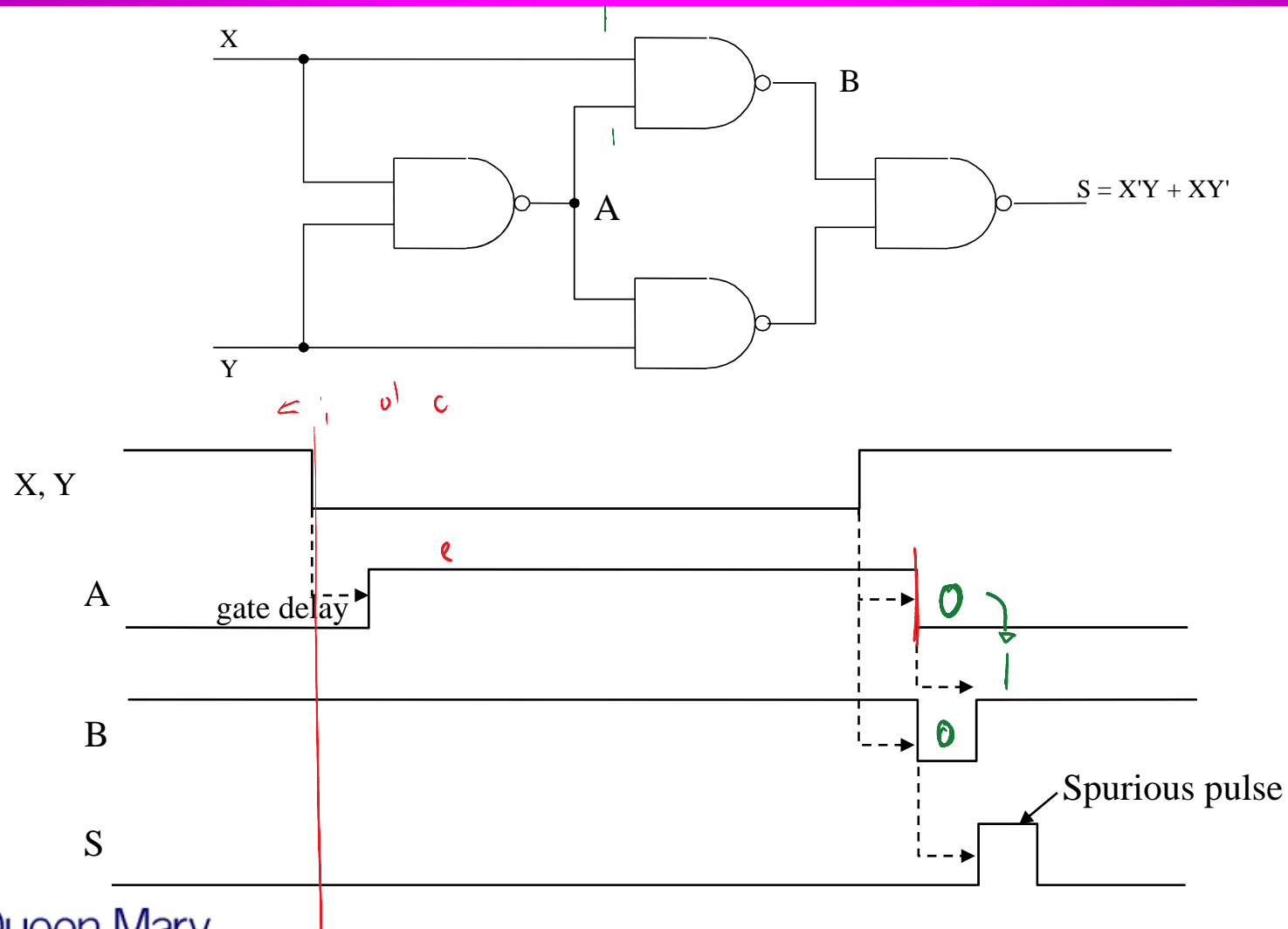

Full Adder

 

$$s = X \oplus Y \oplus c_{in}$$

$$c_{out} = (X.Y) + (X.c_{in}) + (Y.c_{in})$$

Full Adder

C_{in}	X	Y	S	C_{out}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

C_{out} Karnaugh Map

	XY	00	01	11	10
C_{in} 0	0	0	0	1	0
1	0	0	1	1	1

S Karnaugh Map

	XY	00	01	11	10
C_{in} 0	0	0	1	0	1
1	0	1	0	1	0

Full Adder

$$C_{out} = C_{in}.X + C_{in}.Y + X.Y$$

Truth table for C_{out} (Carry Out) as a function of C_{in} (Carry In) and XY (Inputs X and Y):

		XY	00	01	11	10
C_{in}	0	0	0	0	1	0
	1	0	0	1	1	1

Red circles highlight the 1s in the truth table for C_{out} .

$$S = C_{in}'.X'.Y + C_{in}'.X.Y' + C_{in}.Y'.X' + C_{in}.X.Y$$


Truth table for S (Sum) as a function of C_{in} (Carry In) and XY (Inputs X and Y):

		XY	00	01	11	10
C_{in}	0	0	0	1	0	1
	1	1	0	1	0	0


Red circles highlight the 1s in the truth table for S .

Full Adder gate implementations

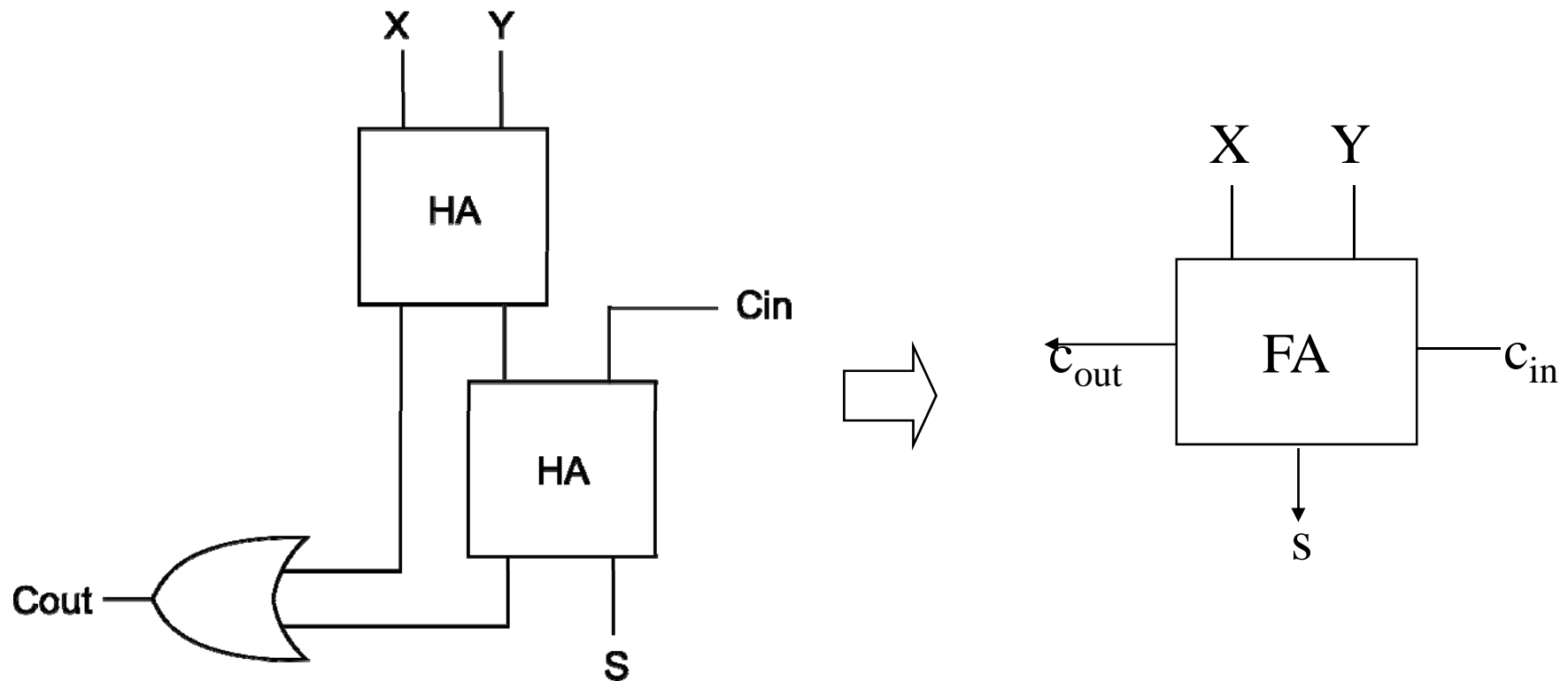Can be implemented with 2 half adders and an OR gate:




Full Adder: NAND-based Ex-OR blocks

 


Consists essentially of two half-adders (XORs with Carry outputs)


4-bit Parallel Adder

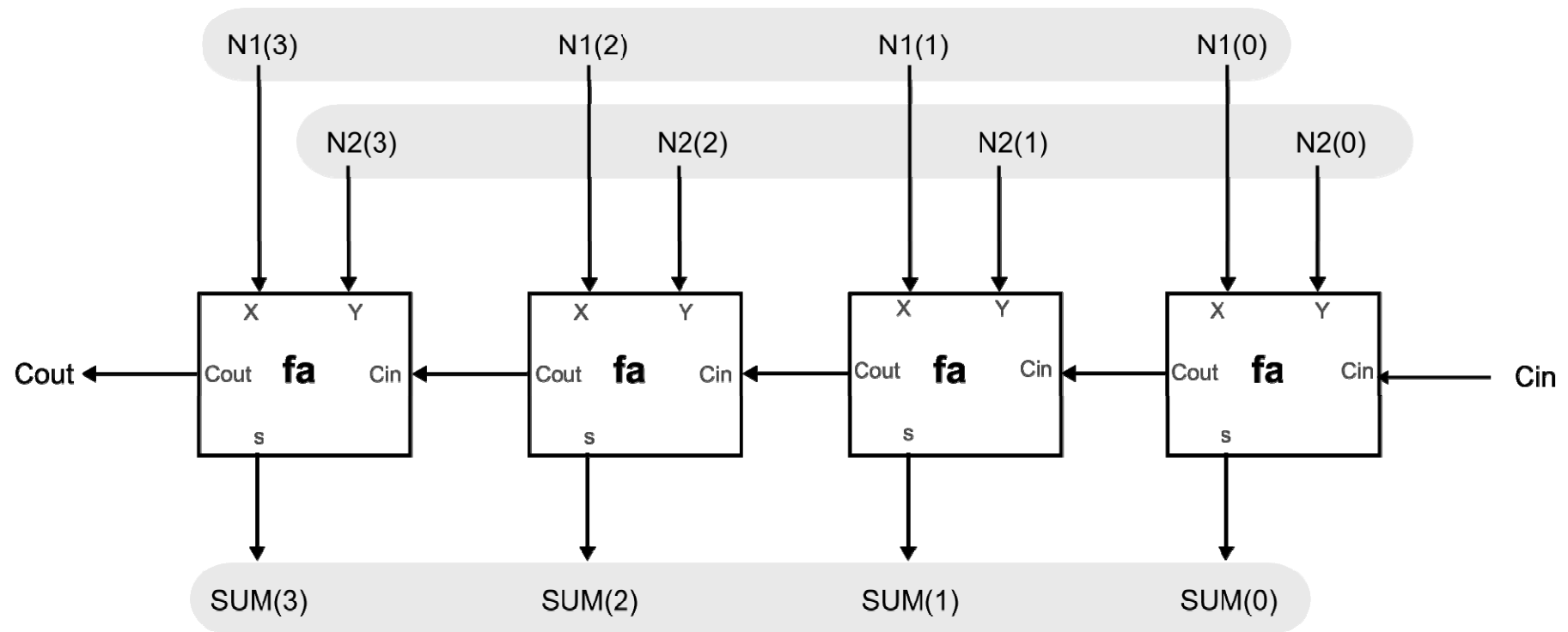

4-bit Parallel Adder

 


Ripple Delay

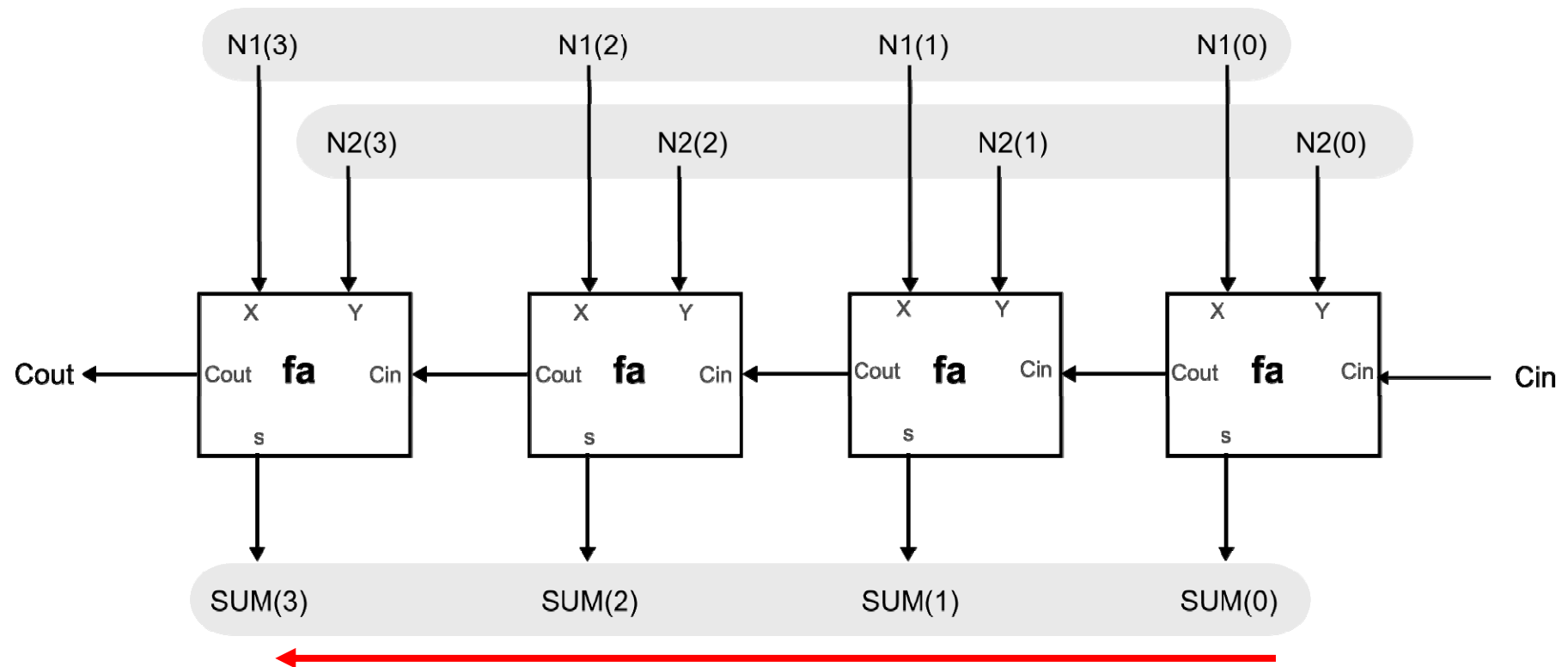


Delay caused by carry outputs at each stage

4-bit Ripple Subtractor using Adders

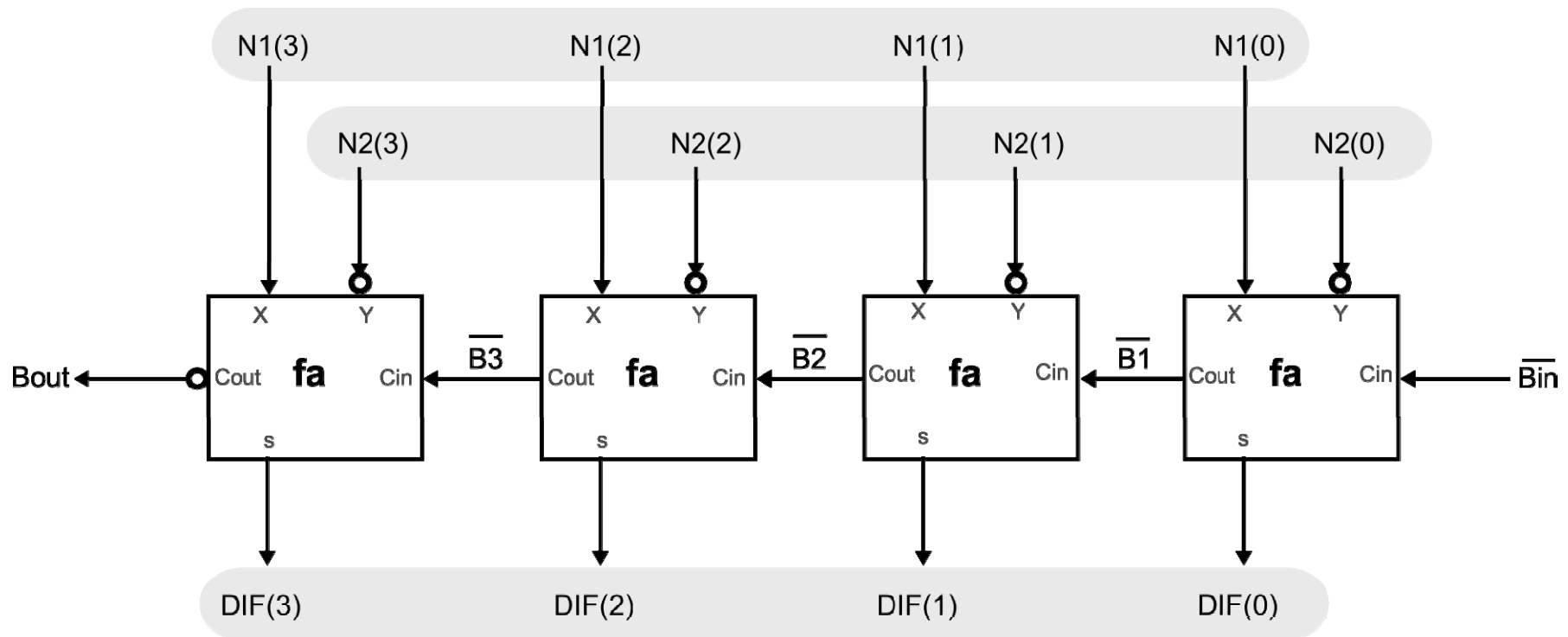


Use two's complement: $A - B = A + (B + 1)$

4-bit Adder/Subtractor

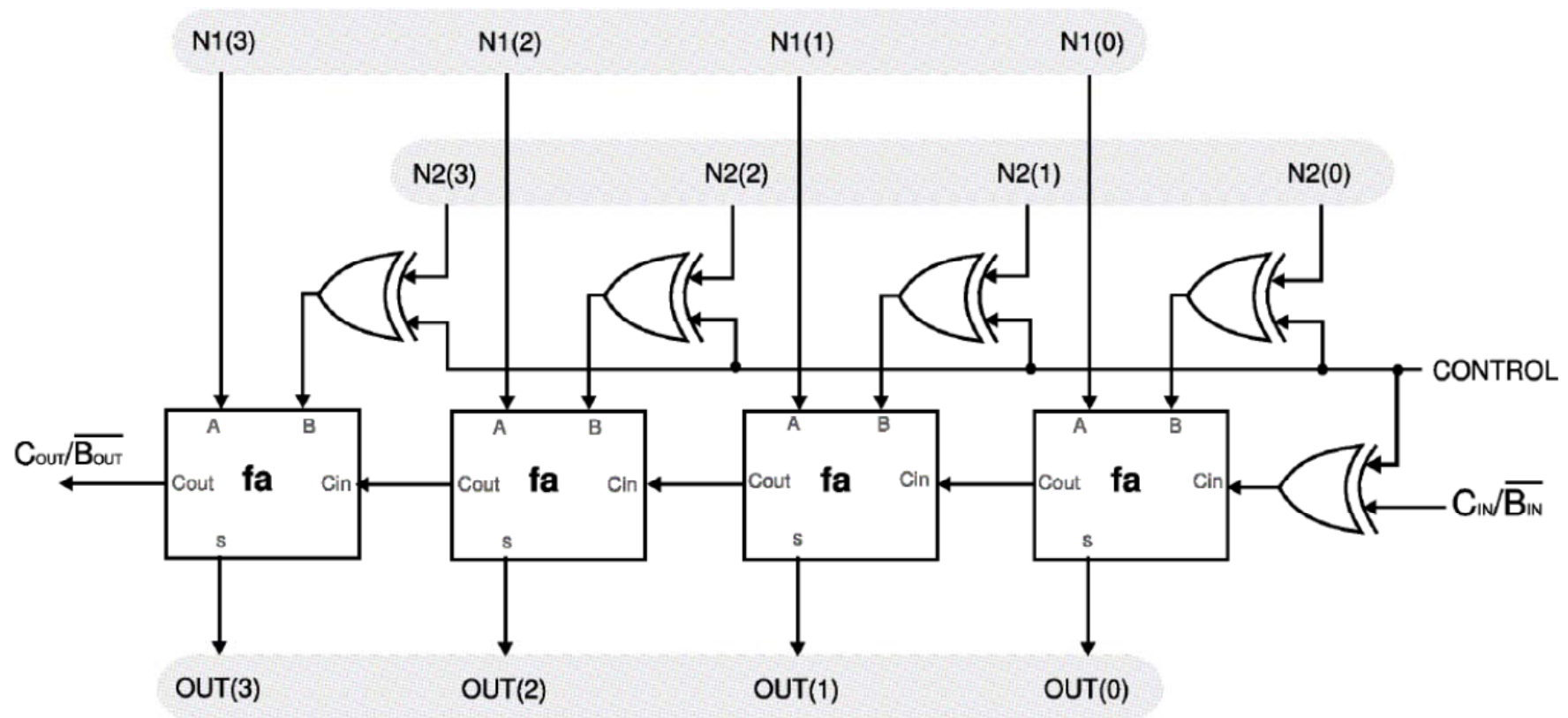


4-bit Adder/Subtractor

 

Control	Output Function
0	Add $(N1 + N2)$
1	Subtract $(N1 - N2)$

An Arithmetic Unit

Control		Arithmetic Function
1	0	
0	0	$A + 1$
0	1	$A + B$
1	0	$A - 1$
1	1	$A - B$

 

An Arithmetic Unit

Can add and subtract
You can also make it increment
and decrement by 1

Control		Arithmetic Function
1	0	
0	0	$A + 1$
0	1	$A + B$
1	0	$A - 1$
1	1	$A - B$

